Prince of Songkla University Facultry of Engineering Department of Computer Engineering

Mid -Term session 1 Year 2002

Date 1 August 2002 Time 9.00-12.00

Subject 240-233 Principles of Digital Systems Room R201

• There are 8 questions. Answer all questions

- All questions are of difference values.
- Calculator, textbooks and hand-out are prohibited.
- Every questions must be clear and show how to get the answer.

NOTE

- All answers must be given in ink.
- Unless otherwise indicated, pencils should only be used for graphical work.


Question	1	2	3	4	5	6	7	8
Scores								


Student ID:	Name:	1
answers. If the (12 marks) (a) The numbusing 5 bit N1 = N2 = - N2 =	ollowing arithmetic operations are considered answer is wrong, the correct answer is are all expressed in a 2's completes plus a sign bit. 010100 101011 010101 = 101001	er must be obtained.
Answer		
(b) -25.25 ₁₀ =	= 11100111.01	
Answer		
(c) $248_8 =$	$2x8^2 + 4x8^1 + 8x8^0$	
Answer		

Student ID:	Name:	2
2. Give the answer: (a) Convert the d	ecimal number 31.87 to num	(12 marks) bers in octal bases
Answer		
(b) Multiply the 2	2' Complement number : 010	010011 x 11000101
Answer		
(c) Divide the bir	nary : 11010 ÷ 11.101	
Answer		

Student ID:	Name:	3
	$A + B[AC + (B + \overline{C})D]$ to standard product - of - (3 marks)	
Answer		
		_
		_
		_
		_
4. Convert the expressions ((A+C)(AB+AC) to standard sum-of-product	_
(SOP) forms.	(3 marks)	
Answer		_
		_
		_
		_
		_

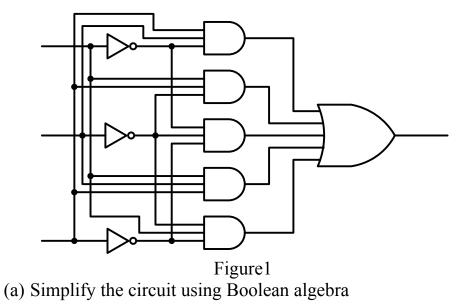
5. Using Figure 1 to answer the following questions (8 marks)



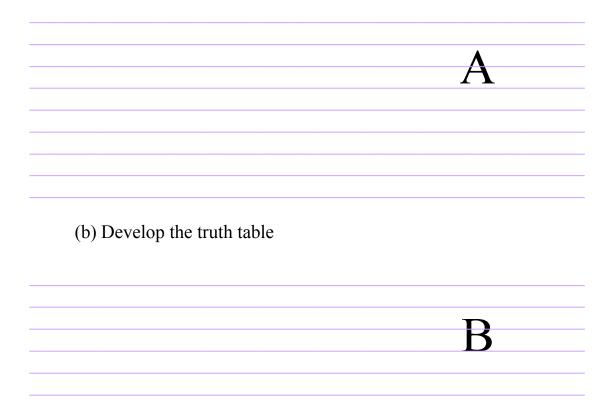

- 6. Use Karnaugh map to simplify the expression (2 marks) $X = \overline{A}B\overline{C}\overline{D} + A\overline{B}\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + AB\overline{C}D + AB\overline{C}D + AB\overline{C}D + AB\overline{C}D$
- 7. In a microcomputer, the microporcessor unit(MPU) is always communicating with one of the following: (1) ramdom-access memory(RAM), which stores programs and data that can be readily changed; (2) read-only memory (ROM), which stores programs and data that never change; (3) external input/output devices (I/O) such as keyboard, video displays, printers and disk drives. As it is executing a program, the MPU will generate an address code that selects which type of device (RAM, ROM, or I/O) it wants to communicate with. Figure 2 shows a typical arrangement where the MPU outputs an eight-bit address code A₁₅ though A₈. Actually, the MPU outputs a 16-bit address code, but the low-order bits A₇ through A₀ are not used in the device selection process. The address code is applied to a logic circuit which uses it to generate the device select signals: RAM, ROM and I/O

(15 marks)

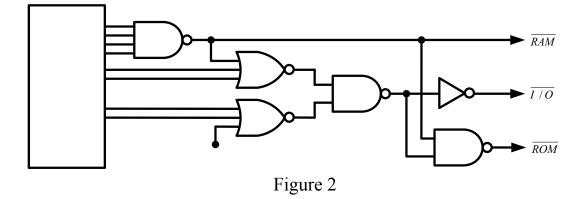

Student ID:	Name:	6
Analyze this o	circuit and determine the following.	
(b) The ran	ge of addresses A_{15} through A_0 that w ge of addresses A_{15} through A_0 that ac	ctivate $\overline{I/O}$
	ge of addresses A_{15} through A_0 that accust be written in Hexadecimal numbers.	

Student ID:		Name:					7
x_1x_0 and y_1y	oresents a multip and produces a ic product of the tiplier.	n outpu	ıt binary	numb	er $z_3 z_2$	$z_1 z_0$ that is	s equal circuit
		ultiplier ircuit	MSB z z z z LSB z	3 2 1 0			
	E.	2					
	F18	gure 3					

Student ID:	Name:	8