 


มหาวิทยาลัยสงขลานครินทร์
คณะวิศวกรรมศาสตร์

สอบปลายภาค: ภาคการศึกษาที่ 2
วันที่สอบ: 27 กุมภาพันธ์ 2548
รหัสวิชา: 240-342
ชื่อวิชา: Logic Circuits Design



ปีการศึกษา: 2547
เวลาสอบ: 9.00-12.00 น.
ห้องสอบ: A201

อ่านรายละเอียดของข้อสอบ และคำแนะนำให้เข้าใจก่อนเริ่มทำข้อสอบ

เวลา: 3 ชั่วโมง (180 นาที)

รายละเอียดของข้อสอบ: ข้อสอบมีทั้งหมด 15 หน้า

- เป็นกระดาษคำถามจำนวน 11 หน้า
- เป็น Datasheet จำนวน 4 หน้า

อนุญาต: เครื่องเขียนต่าง ๆ เช่น ปากกา หรือดินสอ

ไม่อนุญาต: เครื่องคิดเลข หนังสือและสมุดโน้ตใด ๆ เข้าห้องสอบ

คำสั่ง:

- ให้ทำทุกข้อ
- คำตอบทั้งหมดจะต้องเขียนลงในข้อสอบ
- เขียนชื่อและรหัสให้ชัดเจนในข้อสอบทุกแผ่น แผ่นใดไม่เขียนหรือเขียนไม่ครบจะถูกหักคะแนน **1 คะแนน**
- คำตอบส่วนใดอ่านไม่ออก จะถือว่าคำตอบนั้นผิด
- อ่านคำสั่งเพิ่มเติมในแต่ละข้อให้ชัดเจน
- ทุจริตในการสอบมีโทษขั้นต่ำปรับตกในรายวิชานั้นและพักการเรียน 1 ภาคการศึกษา โทษสูงสุดให้ออก

2. จงตอบคำถามต่อไปนี้

- Carry-lookahead adder มีความแตกต่างจากวงจร ripple adder อย่างไรในแง่ของจำนวนเกตและความเร็วของวงจร (3 คะแนน)

.....

.....

.....

.....

.....

- Booth algorithm คืออะไร มีประโยชน์อย่างไร และ กรณีใดที่ Booth algorithm จะมีประโยชน์ในการทำงานสูงสุด (5 คะแนน)

.....

.....

.....

.....

.....

- Carry-Save addition คืออะไรมีประโยชน์อย่างไรจงอธิบายหลักการการทำงานมาพอสังเขป (5 คะแนน)

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

- Multiplicand คืออะไร(0.25 คะแนน)

- Multiplier คืออะไร(0.25 คะแนน)

- Dividerคืออะไร(0.25 คะแนน)


- Dividend คืออะไร(0.25 คะแนน)

- Quotient คืออะไร(0.25 คะแนน)

- Remainder คืออะไร(0.25 คะแนน)

- Summand คืออะไร(0.25 คะแนน)

 4. จากบล็อกไดอะแกรมของวงจร Floating-point addition-subtraction unit ต่อไปนี้ จงออกแบบวงจร SWAP และ วงจร 8-bit subtractor(วงจรที่ล้อมรอบด้วยเส้นประ) ด้วยภาษาวีเอชดีแอล (15 คะแนน)



5. จากซีพียู COE1 ที่นักศึกษาได้เรียนมา หากต้องการสร้าง control unit แบบ Hardwired แล้ว จงออกแบบวงจรสร้างสัญญาณควบคุม INC_PC (12 คะแนน)

คำแนะนำ ให้ดู Datasheet ของซีพียูท้ายข้อสอบประกอบ

- หาสถาปัตยกรรมลอจิกของสัญญาณควบคุม INC_PC (7 คะแนน)

- วาดวงจรสร้างสัญญาณความถี่ INC_PC (5 คะแนน)

6. จากอัลกอริทึมการคูณเลขแบบทั่วไปและแบบ Booth algorithm จงแสดงวิธีการคูณเลขแบบทั่วไป
เปรียบเทียบกับวิธีของ Booth กับตัวเลขที่กำหนดให้(15 คะแนน)

0101101 ตัวตั้ง

0011110 ตัวคูณ

- จงหาค่า Booth recoded multiplier (3 คะแนน).....

.....

.....

- จงแสดงวิธีการคูณเลขแบบทั่วไปพร้อมหาจำนวนครั้งของการบวกของ Summand(3 คะแนน).....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

- จงแสดงวิธีการคูณเลขแบบ Booth algorithm พร้อมหาจำนวนครั้งของการบวกของ Summand(5
คะแนน).....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

Control signal activation of COE1 CPU

Fetching phase for all instructions

Step1 PC_OUT, MAR_IN, RD
 Step2 INC_PC, MDR_IN_F_DATABUS, RD
 Step3 IR_IN, MDR_OUT

1. LD Rx,Ry instruction execution phase

Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, IR_High_in
 Step7 Rx_out, Ry_in, End

2. LD Rx,[Reg16] instruction execution phase

Step4 MAR_IN, RD, Reg16_out
 Step5 MDR_IN_F_DATABUS, RD
 Step6 Rx_in, MDR_out, End

3. LD Ri,#data8 instruction execution phase

Step4 PC_out, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 Ri_in, MDR_out, End

4. Store [Reg16], Rx instruction execution phase

Step4 Reg16_out, MAR_IN, Rx_out, MDR_in
 Step5 MDR_OUT_to_DATABUS, WR
 Step6 MDR_OUT_to_DATABUS, End

5. ADDC Rx,Ry instruction execution phase

Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, IR_High_in
 Step7 Rx_out, TMP1_in
 Step8 ALU_ADD, RY_out
 Step9 Y_out, Rx_in, End

5. SUBB Rx,Ry instruction execution phase

Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, IR_High_in
 Step7 Rx_out, TMP1_in
 Step8 ALU_SUB, RY_out
 Step9 Y_out, Rx_in, End

7. AND Rx,Ry instruction execution phase

Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, IR_High_in
 Step7 Rx_out, TMP1_in
 Step8 ALU_AND, RY_out
 Step9 Y_out, Rx_in, End

8. OR Rx,Ry instruction execution phase

Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, IR_High_in
 Step7 Rx_out, TMP1_in
 Step8 ALU_OR, RY_out
 Step9 Y_out, Rx_in, End

9. IN Ri, port instruction execution phase

Step4 in_port_pin_to_internal_bus, Ri_in, End

10. OUT port,Ri instruction execution phase

Step4 Port_in_f_internal_bus, Ri_out, End

11. NOT Rx instruction execution phase

Step4 Rx_out, ALU_NOT
 Step5 Y_out, Rx_in, End

12. SHR Rx instruction execution phase

Step4 Rx_out, ALU_SHR
 Step5 Y_out, Rx_in, End

13. RL Rx instruction execution phase

Step4 Rx_out, ALU_RL
 Step5 Y_out, Rx_in, End

14. JMP nn instruction execution phase


Step4 PC_OUT, MAR_IN, RD
 Step5 INC_PC, MDR_IN_F_DATABUS, RD
 Step6 MDR_OUT, TMP3_in
 Step7 PC_OUT, MAR_IN, RD
 Step8 INC_PC, MDR_IN_F_DATABUS, RD
 Step9 MDR_OUT, TMP2_in
 Step10 PC_in, TMP2_out, TMP3_out, End

15. JZ nn instruction execution phase


- Step4 PC_OUT, MAR_IN, RD
- Step5 INC_PC, MDR_IN_F_DATABUS, RD
- Step6 MDR_OUT, TMP3_in
- Step7 PC_OUT, MAR_IN, RD
- Step8 INC_PC, MDR_IN_F_DATABUS, RD
- Step9 MDR_OUT, TMP2_in
- Step10 TMP2_out, TMP3_out, if Z=1 then PC_in = 1 else PC_in = 0, End

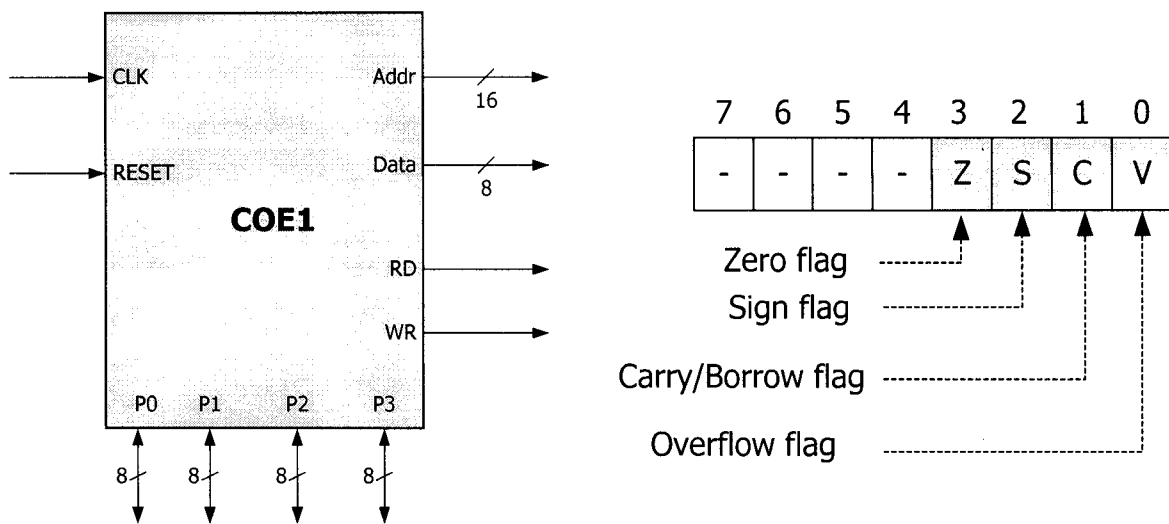16. JC nn instruction execution phase

- Step4 PC_OUT, MAR_IN, RD
- Step5 INC_PC, MDR_IN_F_DATABUS, RD
- Step6 MDR_OUT, TMP3_in
- Step7 PC_OUT, MAR_IN, RD
- Step8 INC_PC, MDR_IN_F_DATABUS, RD
- Step9 MDR_OUT, TMP2_in
- Step10 TMP2_out, TMP3_out, if Cy=1 then PC_in = 1 else PC_in = 0, End



Booth multiplier recoding table

 

Multiplier		Version of multiplicand selected by bit <i>i</i>
Bit <i>i</i>	Bit <i>i</i> - 1	
0	0	0 × M
0	1	+1 × M
1	0	-1 × M
1	1	0 × M

Instruction	Effected flag			Instruction length	Instruction format (1 st -byte.....3 rd -byte)	
	C	Z	V			
ADDC Rx, Ry	Y	Y	Y	2 bytes	01111000	Rx Ry
SUBB Rx, Ry	Y	Y	Y	2 bytes	01111001	Rx Ry
AND Rx, Ry	N	Y	N	2 bytes	01111010	Rx Ry
OR Rx, Ry	N	Y	N	2 bytes	01111011	Rx Ry
LOAD Rx, Ry	N	N	N	2 bytes	01111100	Rx Ry
LOAD Rx, [reg16]	N	N	N	1 byte	0000	Rx reg16
STORE [reg16], Rx	N	N	N	1 byte	0001	Rx reg16
LOAD Ri, #data8	N	N	N	2 bytes	0111101	Ri data8
IN Ri, port	N	N	N	1 byte	0010	port Ri
OUT port, Ri	N	N	N	1 byte	0011	port Ri
NOT Rx	N	N	N	1 byte	0100	Rx
SHR Rx	N	N	N	1 byte	0101	Rx
RL Rx	N	N	N	1 byte	0110	Rx
JMP nn	N	N	N	3 bytes	0111110	nL nH
JZ nn	N	N	N	3 bytes	01111110	nL nH
JC nn	N	N	N	3 bytes	01111111	nL nH

Note:

- Rx, Ry = R0-R7
- Ri = R0, R1
- Port = P0, P1, P2, P3
- Reg16 = R32, R54
- Y = Yes
- N = No