

Department of Computer Engineering

Faculty of Engineering

Prince of Songkla University

Final Examination: Semester I

Academic Year: 2005

Date: 6 October 2005

Time: 9:00-11:00

Subject: 240-440 VLSI System Design

Room: A400

- คำสั่ง**
1. ข้อสอบมีทั้งหมด 5 ข้อ ให้ทำทุกข้อ
  2. อนุญาตให้นำโน้ตขนาด A4 เข้าห้องสอบได้ 1 แผ่น
  3. อนุญาตให้ใช้เครื่องคิดเลขได้ และทำข้อสอบด้วยดินสอหรือปากกา

**ผู้ออกข้อสอบ** ญัตฐา จินดาเพชร

1. 4-input NAND gates in Fig 1(a) and 1(b) have input capacitance of 10 units on each input. It must drive a load of 100 units. Logical effort of 4-input NAND is  $6/3$ , logical effort of 2-input NAND is  $4/3$ , and logical effort of inverter is 1.

 


Fig. 1

- a. Estimate the delay of the NAND gates in Fig 1(a) and 1(b). (10 points)
  - b. Estimate the area represented in the number of total transistor widths of the NAND gates in Fig 1(a) and 1(b). (10 points)
  - c. Discuss which NAND is better and describe the reason (10 points)
2. Design the best speed 2-input NAND gate for the signals A and B as shown in Fig 2. (10 points)

 
 


Fig. 2

3. Show and solve the charge sharing problem for the dynamic 4-input NAND gates. (10 points)
4. Assume a library has modules with delay parameters as shown in Table 1. Design a two-stage loop pipeline sequencing methods as shown in Fig 3.

**Table 1**

Parameter	Description	Delay (ns)
$T_{pd1}$	Logic 1 propagation delay	10
$T_{cd1}$	Logic 1 contamination delay	2
$T_{pd2}$	Logic 2 propagation delay	5
$T_{cd2}$	Logic 2 contamination delay	2
$T_{pcqL}$	Latch Clk-Q propagation delay	2
$T_{ccqL}$	Latch Clk-Q contamination delay	1
$T_{pcqF}$	Flop Clk-Q propagation delay	4
$T_{ccqF}$	Flop Clk-Q contamination delay	1
$T_{pdq}$	Latch D-Q propagation delay	3
$T_{pcq}$	Latch D-Q contamination delay	1
$T_{setup}$	Latch/Flop setup time	1
$T_{hold}$	Latch/Flop hold time	2

 


**Fig. 3**

- a. Determine max-delay and check min-delay constraints for the flip-flop sequencing method. (10 points)
- b. Apply time borrowing technique to speed up the pipeline for the 2-phase latch sequencing method. (10 points)
- c. Discuss throughput of 4a and 4b represented in amount of data samples per second (10 points)


5. Design the following finite state machine by using ROM

(20 points)



Guide: step1: Create state transition table

Present state S1:0	Inputs		Next state S1:0'	Outputs		
	L	R		TR	TL	F
00	0	0	00	0	0	1
00	1	X	01	0	0	1
00	0	1				
01	1	X				
01	0	1				
01	0	0				
10	X	0				
10	X	1				
11	1	X				
11	0	0				
11	0	1				

 

Step 2: Determine sizes of ROM decoder, ROM cell, and Flip-Flops.

Step 3: Map table from step 1 to ROM cell