

มหาวิทยาลัยศรีนครินทร  
คณะวิศวกรรมศาสตร์

สอบกลางภาค : ภาคการศึกษาที่ 1

ปีการศึกษา : 2549

วันที่สอบ : 1 สิงหาคม 2549

เวลาสอบ : 13.30-16.30 น.

รหัสวิชา : 240-440

ห้องสอบ : A203

ชื่อวิชา : VLSI SYSTEMS DESIGN

คำสั่ง: อ่านรายละเอียดของข้อสอบ และคำแนะนำให้เข้าใจก่อนเริ่มทำข้อสอบ

อนุญาต : เครื่องคิดเลข, กระดาษ A4 1 แผ่น ที่เขียนด้วยลายมือ

ไม่อนุญาต : หนังสือ และเอกสารใดๆ เข้าห้องสอบ

เวลา: 3 ชั่วโมง (180 นาที)

คำแนะนำ

- ข้อสอบมี 2 หน้า (รวมใบปะหน้า) 5 ข้อ คะแนนรวม 50 คะแนน
- เขียนคำตอบลงในข้อสอบเท่านั้น
- ใช้ดินสอทำข้อสอบได้ กรณีเขียนไม่ชัดหรืออ่านไม่ออก จะถือว่าคำตอบนั้นผิด
- อ่านคำสั่งในแต่ละข้อให้เข้าใจก่อนลงมือทำ
- อย่าลืม เขียน ชื่อ-นามสกุล และรหัสนักศึกษา ลงในข้อสอบ

ทوجิตในการสอบมีโทษขั้นปรับตกในรายวิชานั้น  
และพักการเรียน 1 ภาคการศึกษา โทษสูงสุดให้ออก

1. Consider the design of a CMOS compound AOI (AND-OR-INVERT)) gate computing  $F = \overline{(A \cdot B) + (C \cdot D)}$ 
  - a. Sketch a transistor-level schematic
  - b. Sketch a stick diagram
  - c. Estimate the area from the stick diagram (unit in  $\lambda$ )
  
2. Sketch a stick diagram for a CMOS gate computing  $Y = A + B + C$  and estimate the cell width and height.
  
3. Calculate the diffusion parasitic  $C_{ab}$  of the drain of a unit-sized contacted nMOS transistor in a  $0.5 \mu\text{m}$  process when the drain is at  $0\text{V}$  and at  $V_{DD} = 5\text{V}$ . Assume the substrate is grounded. The transistor characteristics are  $CJ = 0.42 \text{ fF} / \mu\text{m}^2$ ,  $MJ = 0.44$ ,  $CJSW = 0.33 \text{ fF} / \mu\text{m}$ ,  $MJSW = 0.10$ , and  $\psi_o = 0.75\text{V}$  at room temperature.
  
4. Sketch a 4-input NOR gate with transistor widths chosen to achieve equal rise and fall resistance as a unit inverter. Show why the logical effort is  $9/3$ .
  
5. Consider a process in which pMOS transistors have three times the effective resistance as nMOS transistors. A unit inverter with equal rising and falling delay in this process is shown in Fig.1. Calculate the logical effort of a 2-input NAND gate and a 2-input NOR gate if they are designed with equal rising and falling delay.

 


Fig 1