

PRINCE OF SONGKLA UNIVERSITY
FACULTY OF ENGINEERING

Final Examination: Semester 2

Academic Year: 2549

Date: 24 February 2550

Time: 9.00-12.00

Subject: 211-221 Fundamentals of Electrical Machines

Room: A401, A403

คำสั่ง - ข้อสอบมีทั้งหมด 5 ข้อ

- อนุญาตให้ใช้เครื่องคิดเลข และ Dictionary ได้
- ห้ามนำโน้ต ตำราเรียน เข้าห้องสอบ

-
1. In a 20 kVA 1200/120 V single-phase transformer , the resistance of primary winding is 0.242Ω and the resistance of secondary winding is 0.076Ω . Determine
 - a. the secondary current and primary current
 - b. the equivalent resistance in primary terms.
 - c. the equivalent resistance in secondary terms. (15 คะแนน)
 2. In a 50 kVA 2400/240 V transformer . the core losses and copper losses are 680 W. and 760 W, respectively. Calculate
 - a. The efficiency of this transformer at full load, when the power factor is 0.866 lagging
 - b. maximum efficiency when power factor is 0.866 (15 คะแนน)
 3. A short-circuit test was performed on a 10 kVA 2400/240 V transformer with the following data ;

$$V_{sc} = 138 \text{ V} , \quad I_{sc} = 4.17 \text{ A} , \quad P_{sc} = 202 \text{ W}$$

Calculate ;

- a. The equivalent parameters in primary terms (R_{eH}, X_{eH}, Z_{eH})
- b. The voltage regulation when supplying full load at a power factor 0.866 lagging (20 คะแนน)

4. A three-phase 125 hp 440 V 60 Hz eight-pole Y-connected induction motor has the following electric circuit parameters on a per phase basis referred to stator

$$R_s = 0.068 \ \Omega \qquad X_s = X'_R = 0.224 \ \Omega$$

$$R'_R = 0.052 \ \Omega \qquad X_m = 7.68 \ \Omega$$

The rotational losses are 2400 W. For a slip of 3% determine

- The line current and the power factor
 - The shaft torque
 - The efficiency (25 คะแนน)
5. A 5 hp 220 V 60 Hz four-pole Y-connected three-phase induction motor was tested and the following data were obtained

No-load test : $V_{NL} = 220 \text{ V}$, $P_{NL} = 340 \text{ W}$, $I_{NL} = 6.2 \text{ A}$

Blocked-rotor test : $V_{BR} = 49.4 \text{ V}$, $P_{BR} = 360 \text{ W}$, $I_{BR} = 13.9 \text{ A}$

The dc resistance measurement on the stator winding gives a 4.0 V drop between terminals, when dc current flows 13.9 A. Calculate

- The equivalent parameters(R_e , Z_e , X_e) in stator terms
- The rotational loss
- The efficiency of the motor when operating at a slip of 0.04

(25 คะแนน)

Transformer

no load current $I_0 = I_m + I_w$

$$E_p = 4.44 f N_p \phi_m$$

$$E_s = 4.44 f N_s \phi_m$$

turn ratio $a = \frac{E_p}{E_s} = \frac{N_p}{N_s}$, $\frac{I_s}{I_p} = a$

Equivalent Circuit

$$R_{ep} = R_p + a^2 R_s \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{in primary term.}$$

$$X_{ep} = X_p + a^2 X_s$$

$$R_{es} = R_s + \frac{R_p}{a^2} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{in secondary term.}$$

$$X_{es} = X_s + \frac{X_p}{a^2}$$

Open-circuit test


watt-meter non core losses

Short-circuit Test

$$R_{eH} = \frac{P_{se}}{I_{se}^2} , Z_{eH} = \frac{V_{se}}{I_{se}} , X_{eH} = \sqrt{Z_{eH}^2 - R_{eH}^2}$$

Voltage Regulation
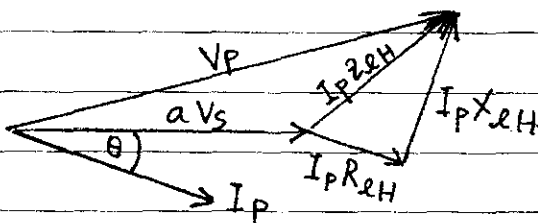
$$\text{voltage regulation} = \frac{V_{no-load} - V_{full-load}}{V_{full-load}} \times 100\%$$



Efficiency

$$\eta = \frac{\text{output power}}{\text{input power}} = \frac{\text{output power}}{\text{output power} + \text{losses}}$$


$$\eta = \frac{kVA_{out} \times PF}{kVA_{out} \times PF + \text{copper losses} + \text{core loss}}$$

The efficiency is maximum when the copper losses equal the core losses

All-day Energy Efficiency

$$\eta_e = \frac{\text{energy output over 24 hours}}{\text{energy input over 24 hours}}$$

Autotransformer

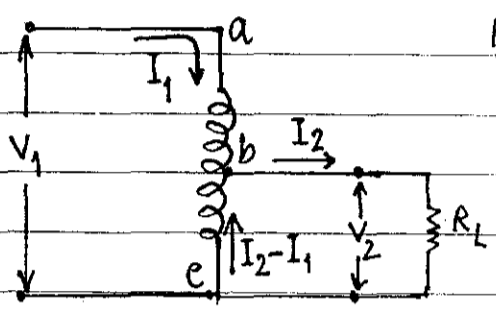

$P_e = V_2 I_1 =$ Conducted power to load through ab

$P_{tr} = V_2 (I_2 - I_1) =$ transformed power to load through bc

Induction Motor

synchronous speed $n_s = \frac{120f}{P}$ r/min

Slip $S = \frac{n_s - n_r}{n_s} \times 100\%$

rotor speed $n_r = (1 - S) \times n_s$ r/min

rotor power input (RPI) = rotor copper loss (RCL) + rotor power developed (RPD)

\therefore RPI (per phase) = $I_R^2 \frac{R_R}{S}$

RCL = $I_R^2 R_R$

RPD = $I_R^2 R_R \frac{1 - S}{S} = RPI (1 - S)$

developed torque $T_d = \frac{RPD}{\omega_r}$ N-m.

\therefore $\omega_r = \frac{2\pi n_r}{60}$ rad/s

shaft torque $T = \frac{RPD - P_{rot}}{\omega_r}$

Maximum Torque


$$S_{mt} = \frac{R'_R}{\sqrt{R_s^2 + (X_s + X'_R)^2}}$$

$$T_{mt} = \frac{RPD_{mt} - P_{rot}}{\omega_{rmt}}$$

$$P_{out} = RPD - P_{rot}$$

P_{rot} = rotational loss = friction, windage and core losses

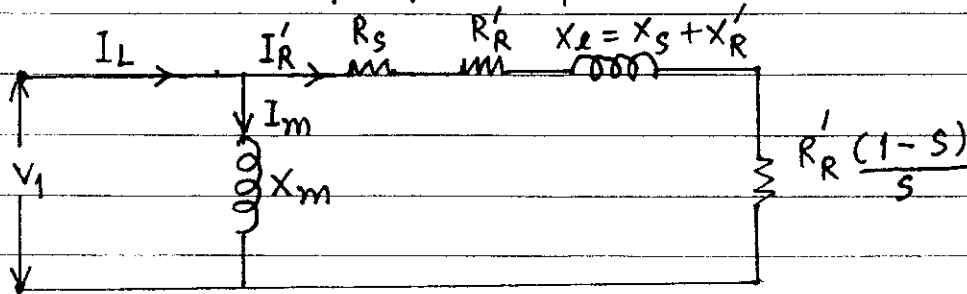Equivalent circuit per phase of Induction motor



เมื่อ stator winding หน่วงโดย Y และให้ค่าขนาดของพิกัด voltage ของมอเตอร์
คือ 220 V. , V_1 คือ phase voltage = $\frac{220}{\sqrt{3}}$ V.


$$I'_R = \frac{V_1}{(R_s + \frac{R'_R}{s}) + j(X_s + X'_R)}$$

$$I_m = \frac{V_1}{jX_m}, \quad I_L = I_m + I'_R$$

Starting Torque

$$T_{st} = \frac{RPI_{st}}{\omega_s}$$

เมื่อ $\omega_s = \frac{2\pi n_s}{60}$

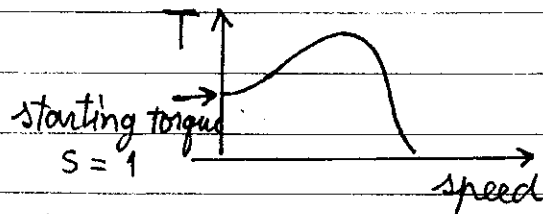

Maximum Torque

$$s_{mt} = \frac{R'_R}{\sqrt{R_s^2 + (X_s + X'_R)^2}}$$

$$T_{mt} = \frac{RPD_{mt} - P_{rot}}{\omega_{rmt}}$$

No-load test

$$P_{NL} = P_c + P_{fr+w} + 3I_{NL}^2 R_s$$

$$P_{rot} = P_{NL} - 3I_{NL}^2 R_s$$

$$\therefore P_{rot} = P_c + P_{fr+w} = \text{friction} + \text{windage} + \text{core losses}$$

$$X_m = \frac{V_{NL}}{\sqrt{3} I_{NL}}$$

Blocked Rotor Test

$$Z_e = \frac{V_{BR}}{\sqrt{3} I_{BR}} = \sqrt{(R_s + R'_R)^2 + j(X_s + X'_R)^2}$$

$$R_e = \frac{P_{BR}}{3 I_{BR}^2} = R_s + R'_R$$

$$X_e = \sqrt{Z_e^2 - R_e^2} = X_s + X'_R$$

$$X_s = X'_R = 0.5 X_e$$