

มหาวิทยาลัยสงขลานครินทร์

คณะวิศวกรรมศาสตร์

การสอบปลายภาค ประจำปีภาคการศึกษาที่ 2

วันที่ 22 กุมภาพันธ์ 2555

วิชา 211-331 Industrial Electronics

ปีการศึกษา 2554

เวลา 13:30-16:30

ห้อง R200

---

คำสั่ง - ให้นำเอกสารประกอบการสอนเข้าห้องสอบได้

- ให้นำเครื่องคิดเลขเข้าห้องสอบได้
- ข้อสอบมีทั้งหมด 4 ข้อให้ทำทุกข้อ

1. Signal-conditioning analysis show that the following equation must relate output voltage to input voltage:

$$V_{\text{out}} = 3.35V_{\text{in}} - 2.68$$

Design circuits to do this using (a) summing amplifier and (b) a differential amplifier

2. Design a voltage-to-current converter that will drive 60 mA into a floating load when the input voltage is 4 V. The input voltage will never go negative. With a  $\pm 12$  V supply, What is the maximum load resistance?

3. Given the circuit of Figure 1, suppose that the op amps are powered with a supply of  $\pm 12\text{ V}$ ,  $R_6 = 100\text{ k}\Omega$ ,  $R_7 = 22\text{ k}\Omega$ , and  $D$  has an avalanche voltage of  $6\text{ V}$ .

Calculate the Circuit Deadband.

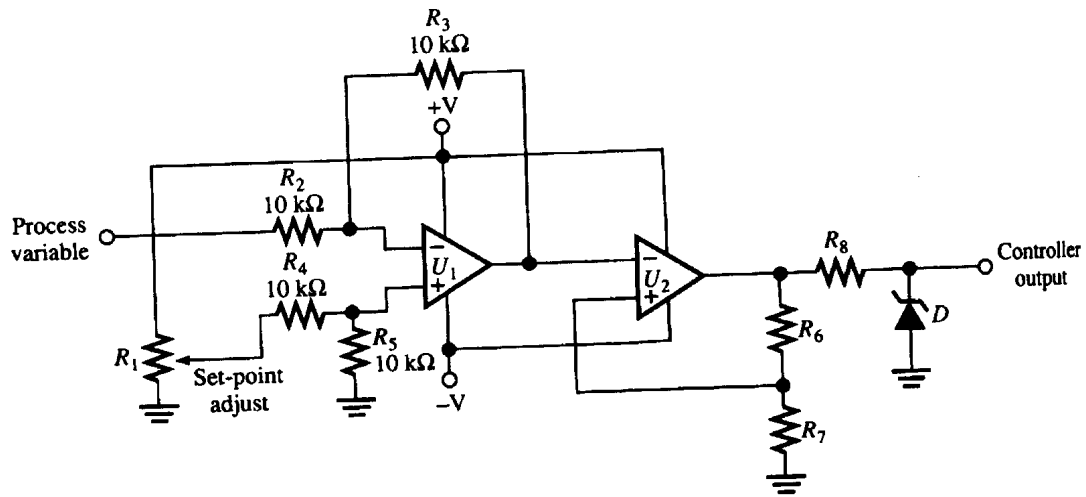


Fig. 1

4. Design a proportional-integral controller with 80% PB and a 0.03-min reset time. Use a 0-5 V input and a 0-12 V output. (See Fig.2)

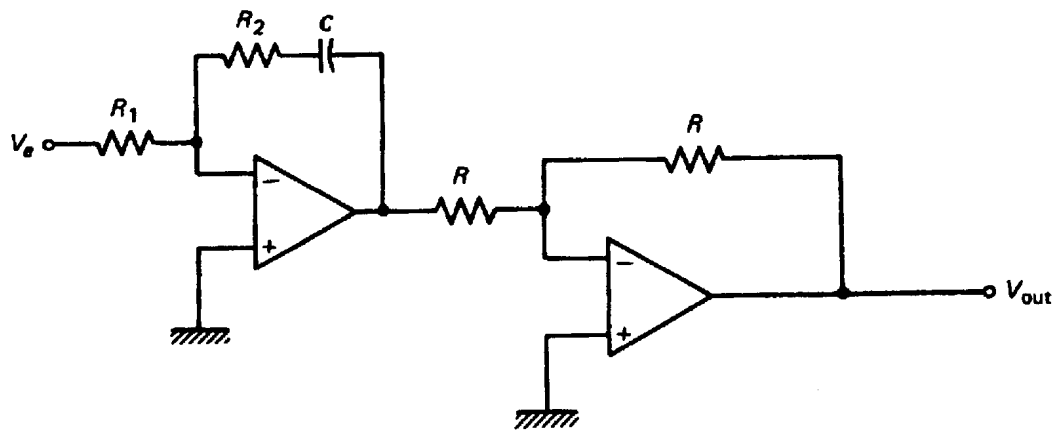


Fig.2