



PRINCE OF SONGKLA UNIVERSITY
FACULTY OF ENGINEERING

Final Examination: Semester 1

Academic Year: 2014

Date: 17 December 2014

Time: 09:00-12:00

Subject: 212-451 Microwave Engineering

Room: A401

-
- ข้อสอบมีทั้งหมด 9 ข้อ ในกระดาษคำถาม 2 หน้า 100 คะแนน
 - ห้ามการหยิบยืมสิ่งใด ๆ ทั้งสิ้น จากผู้อื่น ๆ เว้นแต่ผู้คุมสอบจะหยิบยืมให้
 - ห้ามนำส่วนใดส่วนหนึ่งของข้อสอบออกจากห้องสอบ
 - ผู้ที่ประสงค์จะออกจากห้องสอบก่อนหมดเวลาสอบ แต่ต้องไม่น้อยกว่า 30 นาที ให้ยกมือขออนุญาตจากผู้คุมสอบก่อนจะลุกจากที่นั่ง
 - เมื่อหมดเวลาสอบ ผู้เข้าสอบต้องหยุดการเขียนใด ๆ ทั้งสิ้น
 - ผู้ที่ปฏิบัติเข้าข่ายทุจริตในการสอบ ตามประกาศคณะวิศวกรรมศาสตร์ มีโทษ คือ ปรับตกในรายวิชาที่ทุจริต และพักการเรียน 1 ภาคการศึกษา
 - ให้นักศึกษาสามารถนำสิ่งต่อไปนี้เข้าห้องสอบได้
 - ตำรา
 - เครื่องคิดเลข
 - พจนานุกรม
 - อื่น ๆ
 - หนังสือ
 - กระดาษ A4 ...1... แผ่น
 - ให้ทำข้อสอบโดยใช้
 - ดินสอ
 - ปากกา

ผู้ออกข้อสอบ มณฑล เกียรติวิระสกุล

1. Design a stripline transmission line for a 70Ω characteristic impedance. The ground plane separation is 0.316 cm , and the dielectric constant of the filling material is 2.20 . What is the guide wavelength on this transmission line if the frequency is 3.0 GHz ?

(10 points)

2. A four-port network has the scattering matrix show below.


$$[S] = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

- Is this network lossless?
- Is this network reciprocal?
- What is the return loss at port 1 when all other ports are terminated with matched loads?
- What is the insertion loss and phase delay between ports 2 and 4, when all other ports are terminated with matched loads?
- What is the reflection coefficient seen at port 1 if a short circuit is placed at the terminal plane of port 3, and all other ports are terminated with matched loads?

(20 points)

3. Consider the T-junction of three lines with characteristic impedance Z_1 , Z_2 , and Z_3 , as shown below. Demonstrate that it is impossible for all three lines to be matched, when looking toward the junction.

(10 points)

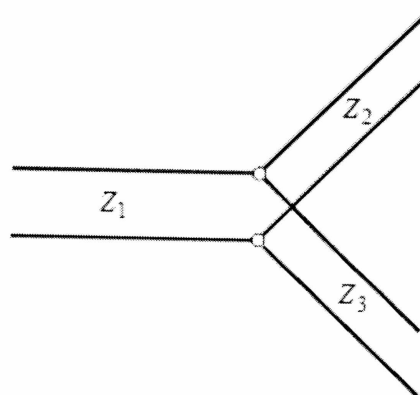

4. Design a single-section quarter-wave matching transformer to match a 350Ω load to a 100Ω line. If the design frequency is 4 GHz, sketch the layout of a microstrip circuit, including dimensions, to implement this matching transformer. Assume the substrate is 0.159 cm thick, with a dielectric constant of 2.2. (20 points)
5. Explain how to construct rectangular waveguides as resonators (4 points)
6. For the RLC circuit, the input impedance is $Z_{in} = \left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C\right)^{-1}$ (10 points)

Derive expressions for the:

- a. P_{in}
 - b. P_{loss}
 - c. W_e
 - d. W_m
 - e. ω_o
 - f. Q and its definition
 - g. BW
7. Dielectric resonators: (6 points)
 - a. What are the important properties of material used for dielectric resonators?
 - b. What are the advantages of dielectric resonator over an equivalent metallic cavity?
 8. Design a Wilkinson power divider with a power division ratio of $P_3/P_2 = 1/3$, and a source impedance of 50Ω . (10 points)
 9. A directional coupler has the scattering matrix given below. Find the directivity, coupling, isolation, and return loss at the input port when the other ports are terminated in matched loads. (10points)

$$\begin{bmatrix} 0.05\angle 30 & 0.96\angle 0 & 0.1\angle 90 & 0.05\angle 90 \\ 0.96\angle 0 & 0.05\angle 30 & 0.05\angle 90 & 0.1\angle 90 \\ 0.1\angle 90 & 0.05\angle 90 & 0.04\angle 30 & 0.96\angle 0 \\ 0.05\angle 90 & 0.1\angle 90 & 0.96\angle 0 & 0.05\angle 30 \end{bmatrix}$$

M. Kiatweerasakul

December 2014

Some useful expressions:

$$\frac{W}{b} = \begin{cases} x & \text{for } \sqrt{\epsilon_r} Z_0 < 120 \Omega \\ 0.85 - \sqrt{0.6 - x} & \text{for } \sqrt{\epsilon_r} Z_0 > 120 \Omega. \end{cases}$$

where

$$x = \frac{30\pi}{\sqrt{\epsilon_r} Z_0} - 0.441.$$

$$\frac{W}{d} = \begin{cases} \frac{8e^{-A}}{e^{2A} - 2} & \text{for } W/d < 2 \\ \frac{2}{\pi} \left[B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right\} \right] & \text{for } W/d > 2. \end{cases}$$

where

$$A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right)$$

$$B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}.$$